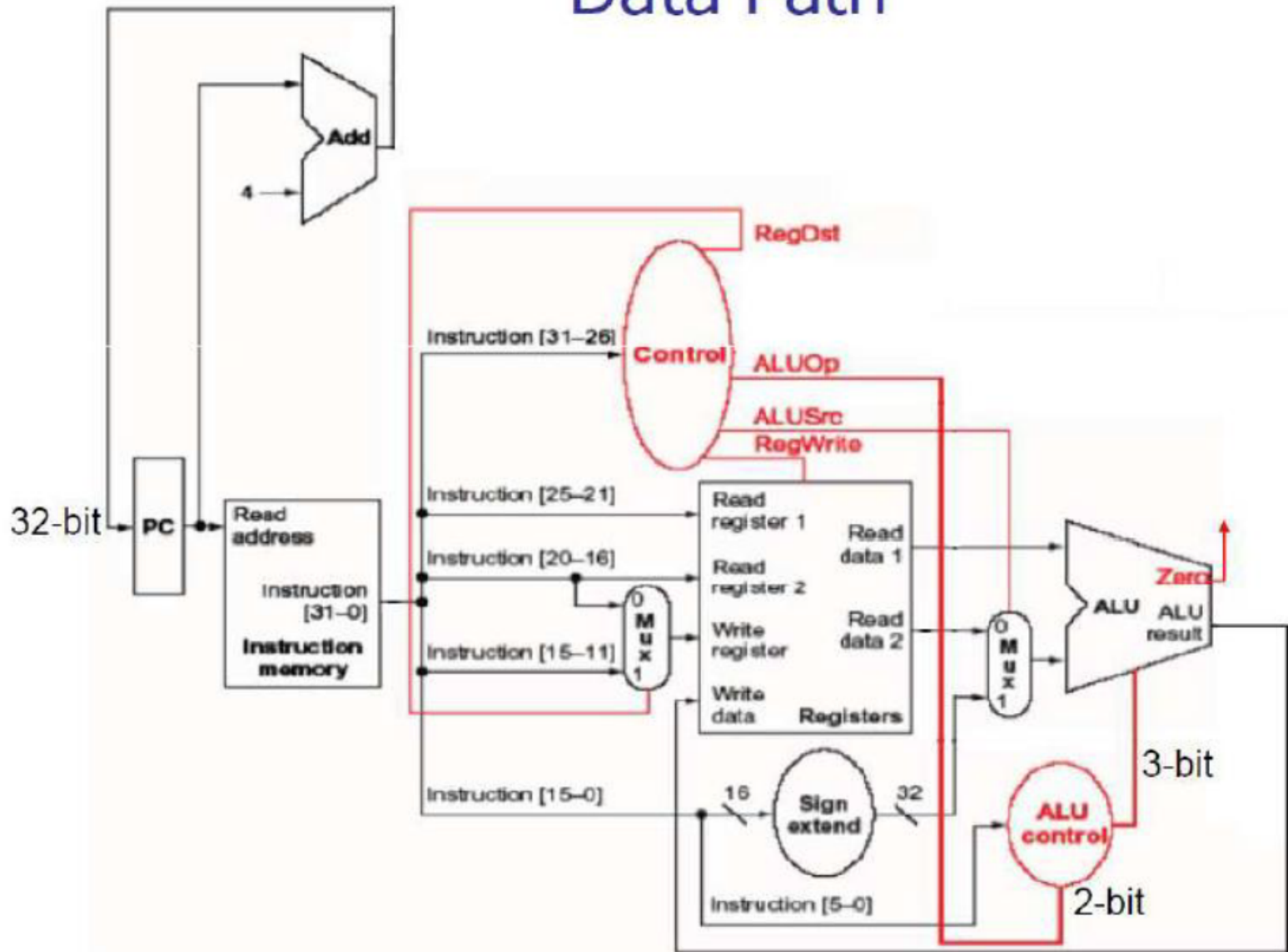


Homework 4

Homework 4: A Single Cycle CPU by Verilog

2017/11/08

Data Path




Requirement #1

- Required Instruction Set
 - and
 - or
 - add
 - sub
 - mul
 - addi


Requirement #2

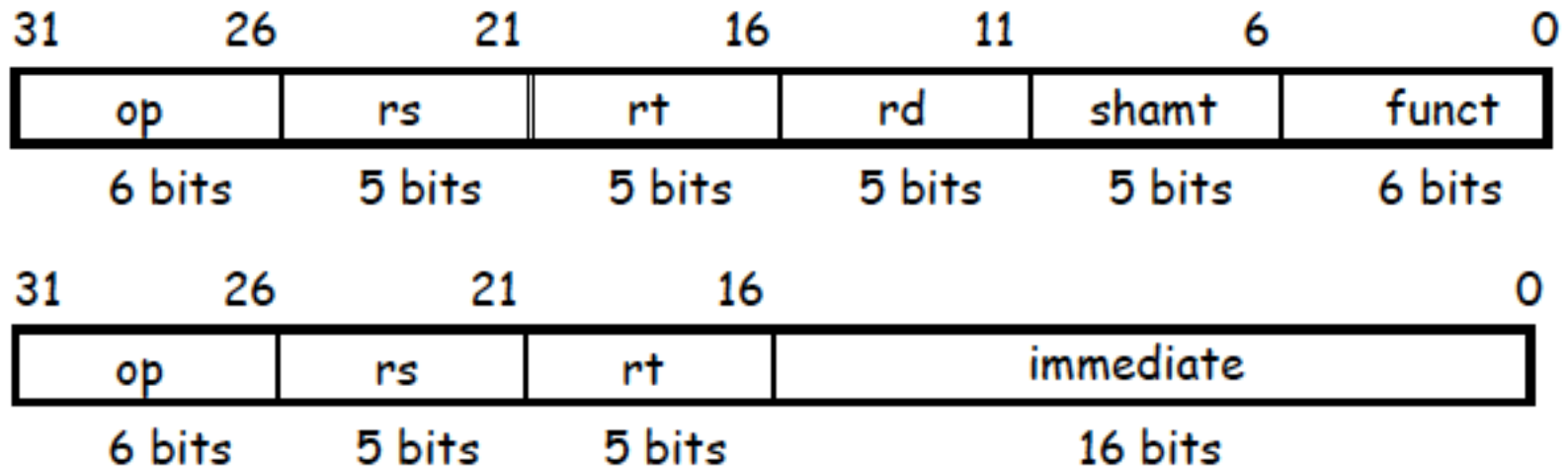- Translate the assembly code to machine code (next page)
- Register file: 32 registers
- Instruction Memory 1KBytes
- Machine code:




Instruction Translation
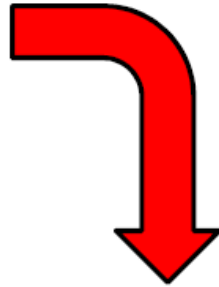
```
add $t0,$0,$0
addi $t1,$0,10
addi $t2,$0,13
mul $t3,$t1,$t1
addi $t1,$t1,1
sub $t2,$t2,$t1
and $t3,$t1,$t2
or $t4,$t2,$t3
```



```
000000_00000_00000_01000_00000_100000 //add $t0,$0,$0
001000_00000_01001_00000000000001010 //addi $t1,$0,10
001000_00000_01010_00000000000001101 //addi $t2,$0,13
000000_01001_01001_01011_00000_011000 //mul $t3,$t1,$t1
001000_01001_01001_00000000000000001 //addi $t1,$t1,1
000000_01010_01001_01010_00000_100010 //sub $t2,$t2,$t1
000000_01001_01010_01011_00000_100100 //and $t3,$t1,$t2
000000_01010_01011_01100_00000_100101 //or $t4,$t2,$t3
```

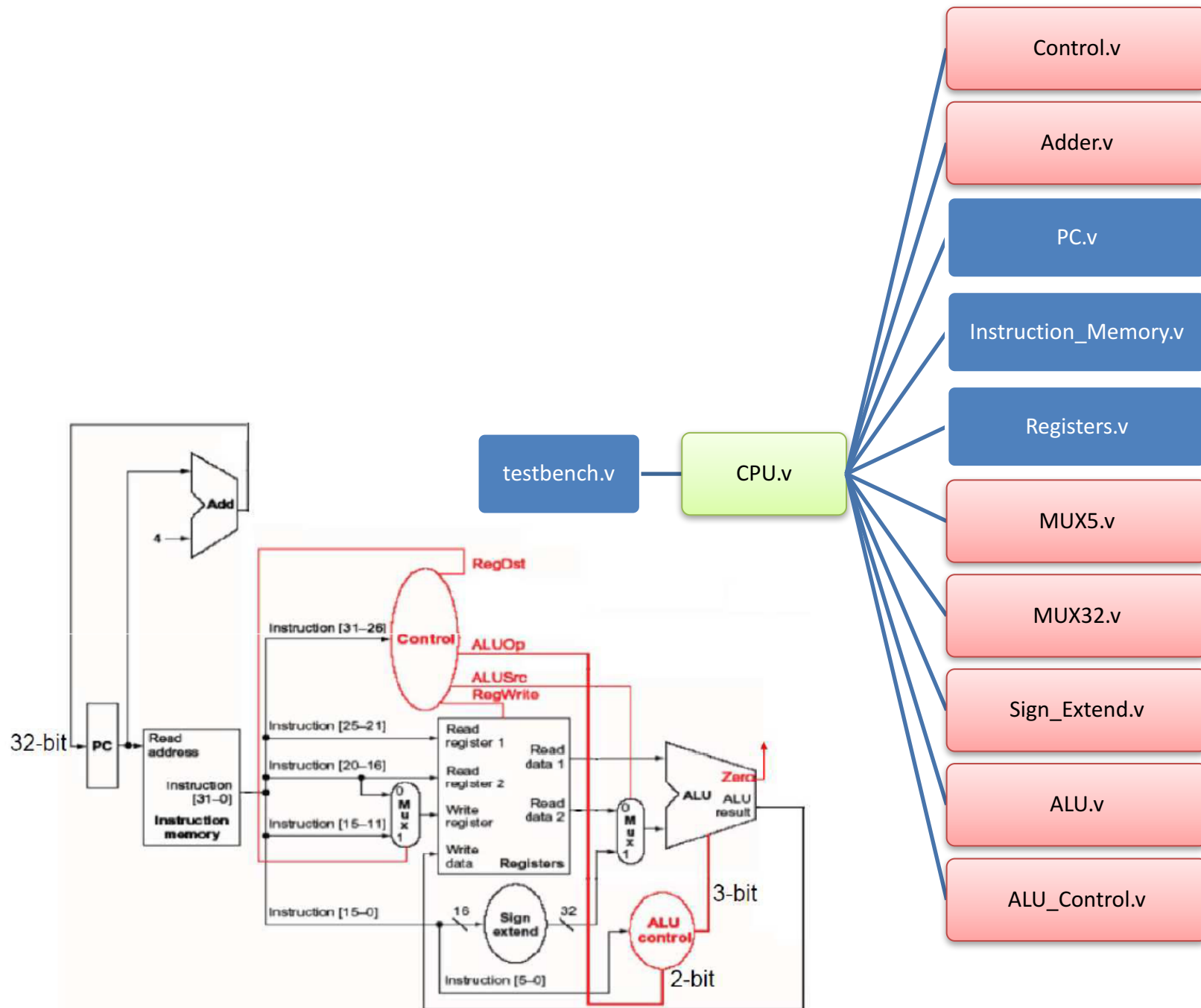

testbench.v

```

CPU CPU(
    .clk_i  (Clk),
    .rst_i  (Reset),
    .start_i(Start)
);

initial begin
    counter = 0;

    // initialize instruction memory
    for(i=0; i<128; i=i+1) begin
        CPU.Instruction_Memory.memory[i] = 32'b0;
    end

    // initialize Register File
    for(i=0; i<32; i=i+1) begin
        CPU.Registers.register[i] = 32'b0;
    end

    // Load instructions into instruction memory
    $readmemb("instruction.txt", CPU.Instruction_Memory.memory);

    // Open output file
    outfile = $fopen("output.txt") | 1;

    Clk = 0;
    Reset = 0;
    Start = 0;

    #(`CYCLE_TIME/4)
    Reset = 1;
    Start = 1;

end

```

CPU.v

```

module CPU
(
    clk_i,
    rst_i,
    start_i
);

// Ports
input          clk_i;
input          rst_i;
input          start_i;

/*
Control Control(
    .Op_i      (),
    .RegDst_o   (),
    .ALUOp_o   (),
    .ALUSrc_o   (),
    .RegWrite_o ()
);
*/

/*
Adder Add_PC(
    .data1_in   (),
    .data2_in   (),
    .data_o     ()
);
*/

PC PC(
    .clk_i      (),
    .rst_i      (),
    .start_i    (),
    .pc_i       (),
    .pc_o       ()
);

```


CPU.v

```
// Ports
input          clk_i;
input          rst_i;
input          start_i;

wire [31:0] inst_addr, inst;

Control Control(
    .Op_i      (inst[31:26]),
    .RegDst_o  (MUX_RegDst.select_i),
    .ALUOp_o   (ALU_Control.ALUOp_i),
    .ALUSrc_o  (/+???*/),
    .RegWrite_o(/+???*/)
);

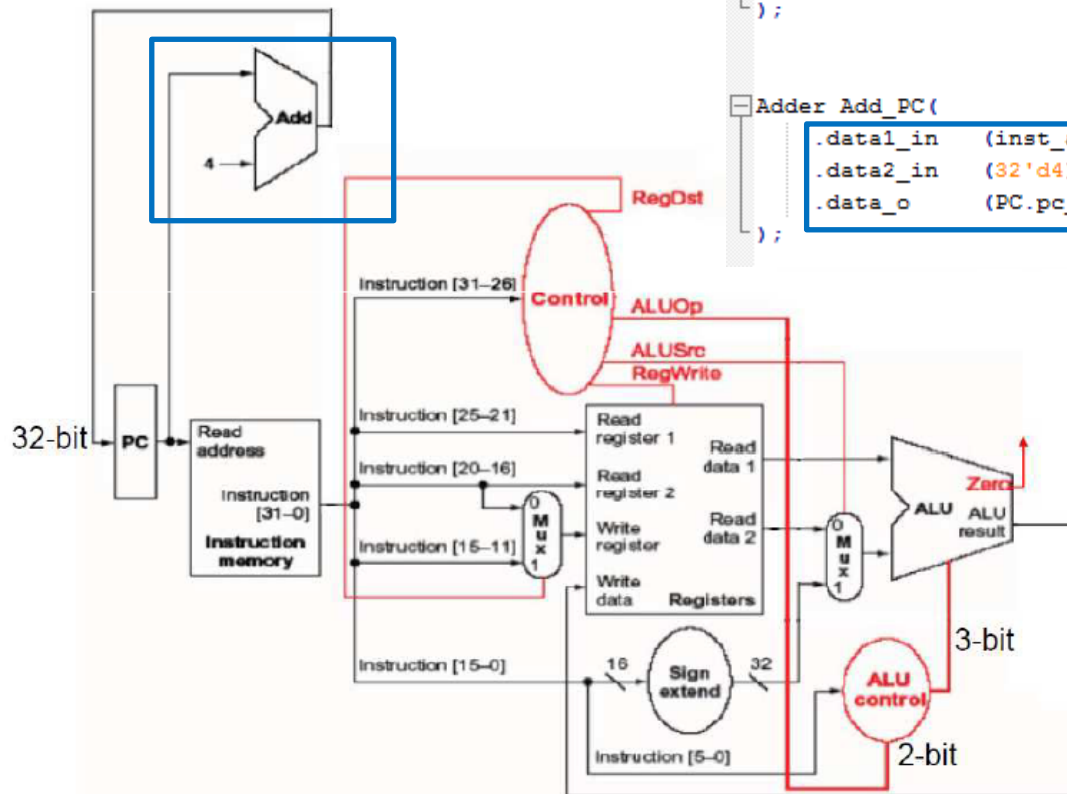Adder Add_PC(
    .data1_in  (inst_addr),
    .data2_in  (32'd4),
    .data_o    (PC.pc_i)
);
```



Adder.v


```
module Adder
(
    data1_in,
    data2_in,
    data_o
);

input [31:0] data1_in, data2_in;
output [31:0] data_o;

assign data_o = data1_in + data2_in;

endmodule
```


Control.v / ALU_Control.v

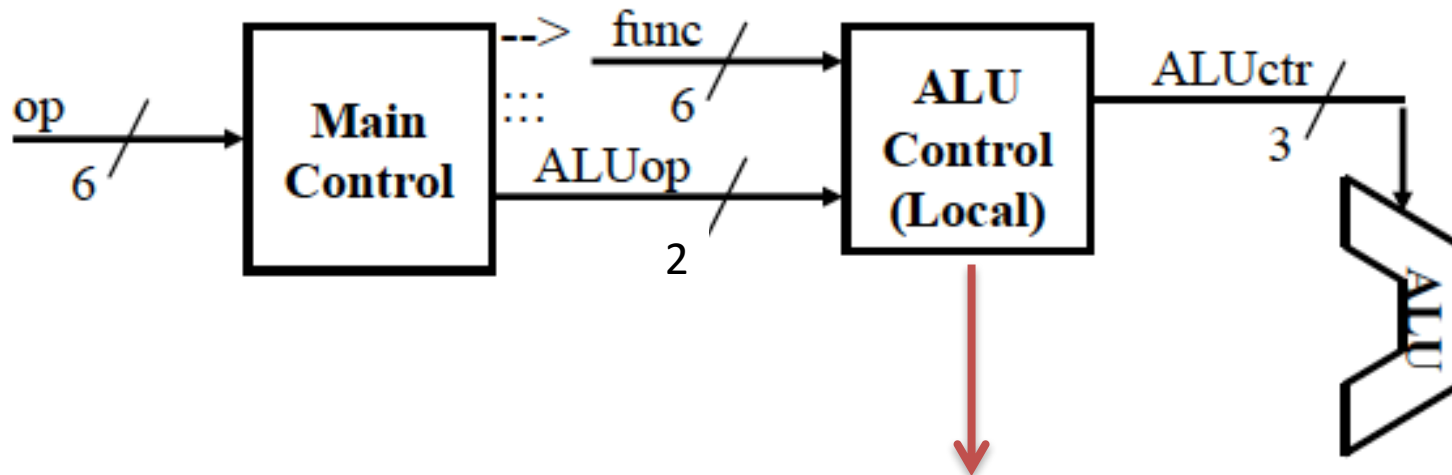

funct<5:0>	Instruction Op.
100000	add
100010	subtract
100100	and
100101	or
011000	mul

Homework 4

- Requirements (1)
 - Source codes (*.v files)
 - testbench.v
 - PC.v
 - Registers.v
 - Instruction_Memory.v
 - CPU.v
 - Adder.v
 - Control.v
 - ALU_Control.v
 - Sign_Extend.v
 - ALU.v
 - MUX32.v
 - MUX5.v
- Requirements (2)
 - Machine Code text file
 - Instruction.txt (no need to modify)
 - There is no need to submit “output.txt”.
 - Report (hw4_b03902xxx.pdf)
 - Coding Environment
 - Module implementation explanation
 - Either English or Chinese is fine
 - (No more than 2 pages)

Homework 4

- Submission format
 - [dir] hw4_b03902xxx_v0
 - hw4_b03902xxx_v0 / hw4_b03902xxx.pdf
 - hw4_b03902xxx_v0 / src / *.v files
- Deadline: 2017/11/20 23:59
- Upload to CEIBA

Homework 4

- Evaluation criteria
 - Report : 15%
 - Code : 85 %
 - Correctness: 36%
 - module correct implementation: 49%
 - Wrong Format: -10%
 - Compile error: coding 0 %
 - Please make sure your code can compile before submitting.